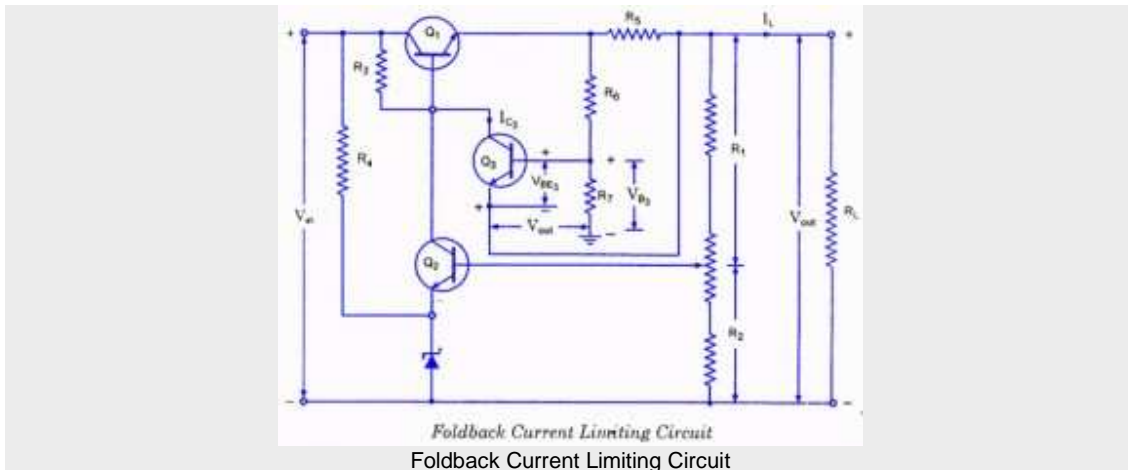


Foldback Current Limiting

A problem with the simple current limiting circuit is that there is a large amount of power dissipation in the series pass transistor Q_1 when the regulator remains short-circuited. This foldback current-limiting circuit is the solution of the above problem.



The circuit of a transistor series voltage regulator with foldback current limiting is illustrated in the figure. In this circuit, the base of transistor Q_3 is biased by a voltage divider network consisting of resistors R_6 and R_7 . The load current I_L flows through resistor R_5 , causing a voltage drop of $I_L R_5$ across it. Thus a voltage of $(I_L R_5 + V_{out})$ acts across the voltage divider $(R_6 + R_7)$ network. The voltage applied to the base of transistor Q_3 is equal to the voltage drop across resistor R_7 and is given as

$$V_{B3} = [R_7 / (R_6 + R_7)] (I_L R_5 + V_{out}) = K(I_L R_5 + V_{out}) \quad [1]$$

$$\text{where } K = R_7 / (R_6 + R_7) \quad [2]$$

The emitter of transistor Q_3 is connected to the positive terminal of V_{out} . Applying Kirchhoff's voltage law to closed mesh of Q_3 shown in the figure we have

$$V_{out} + V_{BE3} = V_{B3} \quad [3]$$

$$\text{or } V_{BE3} = V_{B3} - V_{out} = K(I_L R_5 + V_{out}) - V_{out} = K I_L R_5 - (1-K) V_{out} \quad [4]$$

The magnitude of base drive of transistor Q_1 is controlled by V_{be3} of transistor Q_3 . If the load resistance R_L decreases, the load current I_L will increase, causing voltage drop $I_L R_5$ to increase. This causes V_{B3} to increase and therefore V_{be3} to increase. This makes transistor Q_3 begin to conduct. The increased collector current I_{C3} of transistor Q_3 flows through the resistor R_3 thereby decreasing the base voltage of transistor Q_1 . This results in reduction of the conduction level of

transistor Q₁, limiting further increase in load current I_L . Using the base-emitter saturation voltage $V_{BE3} = 0.7$ volts, the maximum current is

$$I_{Lmax} = [0.7 + (1-K) V_{out}] / KR_5 \quad [5]$$

Example for non-foldback current limiting

For $R_5 = 1$ ohm and $K = 1$, $I_{Lmax} = 0.7$ amps (independent of V_{out})

Example for foldback current limiting

For $R_5 = 1$ ohm, $V_{out} = 5$ volts, and $K = 0.7$, $I_{Lmax} = 3.1$ amps.

For $R_5 = 1$ ohm, $V_{out} =$ short circuit, and $K = 0.7$, $I_{Lshort} = 1.0$ amps.

Check the actual I_{Lmax} and I_{Lshort} by varying R_5 and bench test it.

One final note. In Eq [4], for $I_L=0$, $V_{BE3} = - (1-K) V_{out}$. Thus the base emitter junction is reverse biased when the load current is zero. The V_{EBO} rating of most transistors is very low, sometimes about 5 volts. A properly placed diode can protect this junction.

=====

Adapted from <http://www.circuitstoday.com/category/power-supplies/page/2>

By Bob S 12/26/2010